

INDIAN MARITIME UNIVERSITY
(A CENTRAL UNIVERSITY, GOVT. OF INDIA)

SEMESTER- I, B.TECH. (MARINE ENGINEERING) – JUNE 2014 EXAMS

BASIC ELECTRICAL AND ELECTRONICS ENGINEERING (T 1104/ T 2104)

Time:- 3 Hrs
Date: 26.06.2014

Max Marks : 100
Pass Marks : 50

PART - A
Compulsory Questions

(10 X3 = 30 Marks)

1. (a) The sticker on a compact disc player says that it draws 288 mA of current when powered by a 9 V battery. What is the power of a CD player?
- (b) Define a network and a node.
- (c) What is called magnet? How it is classified?
- (d) Define Impedance.
- (e) Write down the instantaneous voltage equation and draw the phasor diagram for three – phase system.
- (f) Define illumination.
- (g) What is called semiconductor? How it is classified.
- (h) What is Zener Diode? Draw the characteristics curve for a zener diode and label it.
- (i) What is called rectifier? Draw the output waveform of half wave rectifier.
- (j) Why NPN transistor is most widely used?

PART - B

(5 X14 = 70 Marks)

Answer Any Five of the following

2. (a) Discuss Kirchhoff's Current law and Voltage law with neat sketch and necessary equations. (7)
- (b) Explain briefly about electro static induction with neat sketch. (7)
3. (a) Draw hysteresis loop and explain briefly the various parts on it. (7)
- (b) Two 200 turn, air cored solenoids, 25 cm long have a cross sectional area of 3 cm^2 each. The mutual inductance between them is $0.5 \mu\text{H}$. Find the self inductance of the coils and the coefficient of coupling. (7)

4. (a) A sinusoidal voltage $v = 50 \sin \omega t$ is applied to a series RL circuit. The current in the circuit is given by $i = 25 \sin (\omega t - 53^\circ)$. Determine the (7)
- (i) Apparent Power (ii) Average Power and (iii) Power factor.
- (b) A 100 V, 50 Hz supply is applied across the series circuit consisting of $R = 10 \Omega$, $L = 1 \text{ mH}$, and $C = 20 \mu\text{F}$. Find the input current and voltage across each element. (7)
5. (a) What is called transducer? How it is classified? What are the basic requirements of a transducer? (2 + 1 + 4)
- (b) A 230 V single phase energy meter has a constant load current of 10 A at unity power factor. If the aluminum disc in the meter is meter makes 1200 revolutions in 3 hours, calculate the energy meter constant in revolutions per kwh. (7)
6. (a) Distinguish among Intrinsic and Extrinsic semiconductor. (7)
- (b) What is a diode? How depletion layer is formed in diode? (2 + 5)
7. (a) Differentiate between avalanche breakdown and zener breakdown. (7)
- (b) Write a short note on photoelectric emission and electric field emission. (7)
8. Explain the input and output characteristics of a transistor in common base configuration. (14)
9. (a) Explain the working principle of full wave bridge rectifier with neat sketch. (7)
- (b) Discuss diode clamper with neat sketch. (7)
