

7413

INDIAN MARITIME UNIVERSITY
(A CENTRAL UNIVERSITY, GOVERNMENT OF INDIA)
B.TECH (MARINE ENGINEERING)
DECEMBER 2014 / JANUARY END SEMESTER EXAMINATION
III SEMESTER
ELECTRONICS (T-2302 / T 1302)

Time : 03.00 Hrs

Max Marks : 100

Date: 24-12-2014



Pass Marks : 50

PART- A (3 × 10 = 30 Marks)
Compulsory Questions

1. 3x10= 30

a) Describe the operation of J-K-flip-flop with State diagram. 3

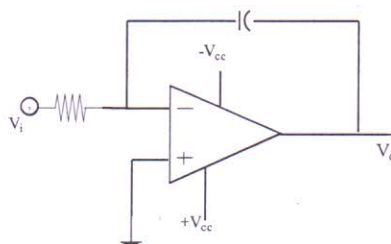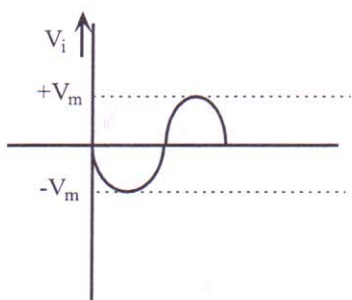b) If input to the circuit shown below is 3



c) Implement the function with 4:1 MUX 3

$$f(A, B, C) = \sum (1, 2, 4, 7)$$

d) Minimize the function using K-map 3

$$f(A, B, C, D) = \sum (0, 2, 4, 5, 8, 9, 11) \text{ \& don't care } = (3, 7, 10, 15).$$

e) Find the equivalent *gray code* of given binary numbers 10101, 11101 3

f) List the *ideal characteristic* of an OP-AMP. 3

g) Discuss the advantages of SSB system in radio telephony. 3

h) State the advantages of negative feedback 3

i) Why self bias is more desirable than fixed bias for transistor biasing? 3


j) Chose the correct alternative: The colour of the spot on the screen of a CRO depends on 3

- (1) Intensity of electron beam (2) Frequency of the deflection voltage
 (3) Coating material of the screen

PART - B (5x14 = 70 Marks)

Answer any five from the following eight questions

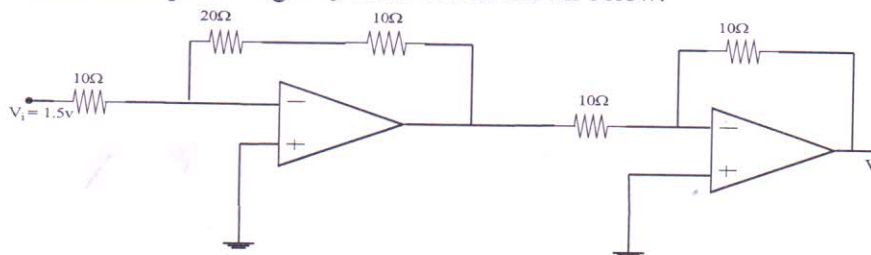2. ✓
- a. Design a BCD adder circuit. Draw the logic circuit diagram. 7
- b. Briefly discuss the construction and working of *4-bit shift register*. Also show the *Timing Diagram* of the counter. 7
- 3.
- a) Design a *BCD to 7-segment decoder*. 10
- b) Realize a two input *NOR GATE* using TTL and briefly discuss its operation. 4
- 4.
- a. What is *Input offset current*. How effect of Input offset current is compensated in op-amp 7
- b. Find the output voltage V_o of the circuit shown below. 7



5. ✓
- a. How can signal are classified in 8085 microprocessor. Describe briefly accumulator register 8
- b. Draw and explain CRO 6
6. ✓
- a. Draw and explain operational principle of any Thyristors 7
- b. What are the advantages of a negative feedback and Draw and explain class A Amplifier. 7

7.

- a. Explain with diagram for MOSFET 7
- b. A germanium transistor has a collector cut off current $I_{CBO} = 14 \mu A$ at 7
room temperature and $\beta = 50$. It is used in common emitter amplifier.
(1) Calculate the collector current when the base current is 0.2 mA.
(2) Assuming β does not change with temperature, find the new collector
current, if the temperature of the transistor rises through 50° .

8.

- a. Draw a fixed biased circuit. Explain why the circuit is unsatisfactory if 7
the transistor is replaced by another of the same type.
- b. Explain Wine bridge Oscillator 7

21
15
12
10
8
6
4
2